 


**Introduction to Digital Design**  
**SAMPLE FINAL EXAM**  
 - Solutions -

**Problem 1.** (10 points)

a) Give a state diagram and state/output table of a Mealy machine which implements the following behavior:

$$z(t) = \begin{cases} x'(t) & \text{if } x(t) = 0 \text{ and } x(k) = 0 \text{ for all } k < t \\ 0 & \text{if } x(t) = 1 \text{ and } x(k) = 0 \text{ for all } k < t \\ x(t) & \text{otherwise} \end{cases} \quad (1)$$



PS	x=0	x=1
S0	S0,1	S1,0
S1	S1,0	S1,1
	NS,z	

b) Illustrate the time behavior for the input sequence shown bellow. Assume that  $x(k) = 0$  for  $k < 0$ .

$t$	0	1	2	3	4	5	6
$x(t)$	0	0	1	0	1	1	0
$z(t)$	1	1	0	0	1	1	0

c) Is this a finite-memory system? Explain your answer.

No; the output cannot be determined from the last  $m$  inputs for any fixed integer  $m$ .

**Problem 2.** (8 points)

Find an equivalent finite state machine with a minimum number of states. Show all partitions and the minimal state table.

$PS$	$x = 0$	$x = 1$
A	E,0	C,0
B	C,0	A,0
C	B,0	G,0
D	G,0	A,0
E	F,1	B,0
F	E,0	D,0
G	D,0	G,0

The partitions are:

$$P1 = (A \ B \ C \ D \ F \ G)(E)$$

$$P2 = (A \ F)(B \ C \ D \ G)(E)$$


$$P3 = (A \ F)(B \ D)(C \ G)(E)$$

$$P4 = (A)(F)(B \ D)(C \ G)(E) = P5$$

The minimal state table is:

$PS$	$x = 0$	$x = 1$
A	E,0	C,0
B	C,0	A,0
C	B,0	C,0
E	F,1	B,0
F	E,0	B,0

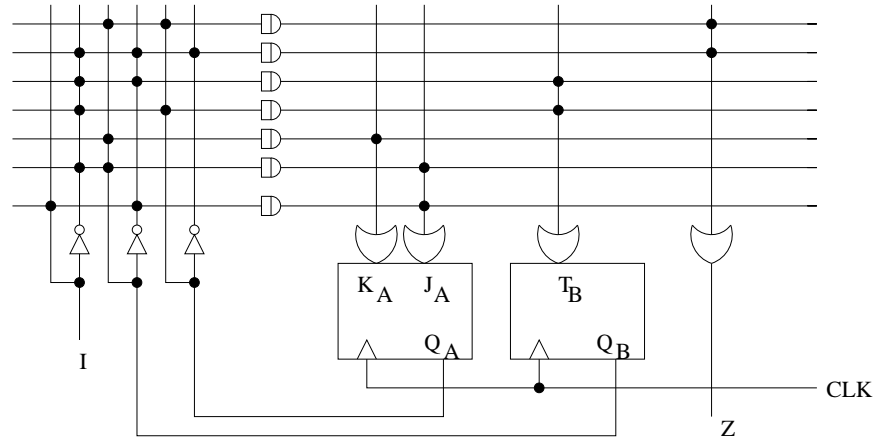**Problem 3.** (10 points) Derive the state transition/output table for the implementation of the finite state machine shown in the figure below. The next state and output functions are implemented by a PLA structure. The machine has one input  $I$  and one output  $Z$ . Show expressions for the flip-flop inputs.



$$J_A = Q_B I' + Q'_B I$$

$$K_A = Q_B$$

$$T_B = Q'_B I' + Q_A I'$$

$$Z = Q_A Q_B + Q'_A Q'_B I'$$

PS( $Q_A Q_B$ )	I	$J_A$	$K_A$	$T_B$	NS	Z
00	0	0	0	1	01	1
00	1	1	0	0	10	0
01	0	1	1	0	11	0
01	1	0	1	0	01	0
10	0	0	0	1	11	0
10	1	1	0	0	10	0
11	0	1	1	1	00	1
11	1	0	1	0	01	1

**Problem 4.** (14 points) (a) Design a cyclic counter with the output sequence 0, 1, 3, 7, 6, 4, 0, 1, ... (of period 6) using JK flip-flops and AND, OR, NOT gates if needed. Assume that the input  $x = 1$  always. Select a state assignment that is the same as the coding for the output, that is  $z(t) = s(t)$ . Show the state/output table. Minimize all expressions. Show the logic diagram of the counter.

State/output table:


PS	NS	$J_2 K_2$	$J_1 K_1$	$J_0 K_0$
000	001	0-	0-	1-
001	011	0-	1-	-0
010	—	—	—	—
011	111	1-	-0	-0
100	000	-1	0-	0-
101	—	—	—	—
110	100	-0	-1	0-
111	110	-0	-0	-1

		Q0			
J <sub>2</sub>		0	0	1	-
Q2		-	-	-	-
		Q1			
		Q0			
K <sub>2</sub>		-	-	-	-
Q2		1	-	0	0
		Q1			


		Q0			
J <sub>1</sub>		0	1	-	-
Q2		0	-	-	-
		Q1			
		Q0			
K <sub>1</sub>		-	-	0	-
Q2		-	-	0	1
		Q1			

		Q0			
J <sub>0</sub>		1	-	-	-
Q2		0	-	-	0
		Q1			
		Q0			
K <sub>0</sub>		-	0	0	-
Q2		-	-	1	-
		Q1			


 
$$J_0 = Q'_2 \quad K_0 = Q_2 \quad J_1 = Q_0 \quad K_1 = Q'_0 \quad J_2 = Q_1 \quad K_2 = Q'_1$$



 **Problem 4 (cont.)** (b) Design the cyclic counter defined in part (a) using the "one flip-flop per state" approach with D flip-flops. To obtain the output, use a 8-input binary encoder. Show all connections. How is the counter initialized?



**Problem 5.** (10 points) Design a combinational network that finds the largest and the second largest of four nonnegative integers  $A, B, C, D$ . Each integer is represented by four bits. You may use only the following module types:  $4 \times 2$ -input multiplexer and four-bit comparator. The two-bit output of the comparator is  $z = (z_1, z_0)$ . If the first integer is larger than the second, the output is  $z = 10$ . If the second number is larger, the output is  $z = 01$  and if the numbers are equal, the output is  $z = 00$ ). Indicate all inputs and connections on the modules being used.

  

**Problem 6.** (8 points)

a) Complete the following table assuming true-and-complement number systems. If there is a problem in completing the table, explain. All implicit and explicit values are given in the decimal number system.

Number system	Number of digits $n$	Signed integer $x$	Representation value $x_R$	Digit-vector $X$
2's compl.	7	-39	89	1011001
1s' compl.	8	-89	167	10100111
2's compl.	9	-220	292	100100100
2's compl.	6	-43	NA	NA

b) Compute  $z = a + 2b - c$  in 2's complement for  $a = -7$ ,  $b = 12$ , and  $c = -97$ . Perform calculations on bit-vectors representing  $a$ ,  $b$  and  $c$  and show every step of your work. How many bits should  $z$  have to represent the correct result? Check your work by showing, for each step, the corresponding values in decimal number system.

a =	111001	(-7)
b =	001100	(12)
2b =	011000	(24)
c =	10011111	(-97)
a+2b =	010001	(17)
z=a+2b-c =	01110010	(114)


The result  $z$  has 8 bits.




**Problem 7.** (10 points)

a) Design a 4-bit by 2-bit multiplier module M42. The operands are positive: the multiplicand is  $X = (x_3, x_2, x_1, x_0)$ , the multiplier is  $Y = (y_1, y_0)$ , and the product  $p = (p_5, \dots, p_0)$ . You are allowed to use AND gates, full-adders (FA) and half-adders (HA) only.

		$x_3$	$x_2$	$x_1$	$x_0$
				$y_1$	$y_0$
		$x_3 y_0$	$x_2 y_0$	$x_1 y_0$	$x_0 y_0$
		$x_3 y_1$	$x_2 y_1$	$x_1 y_1$	$x_0 y_1$
$p_5$	$p_4$	$p_3$	$p_2$	$p_1$	$p_0$

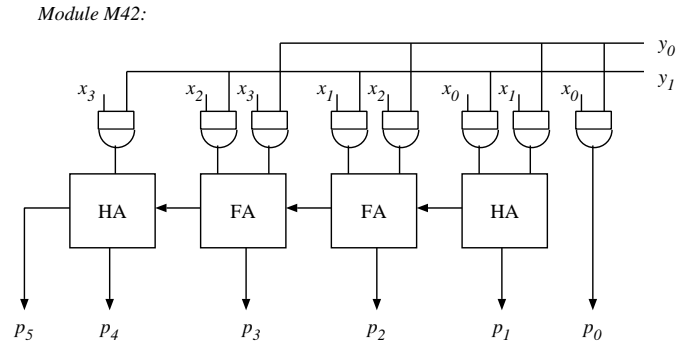

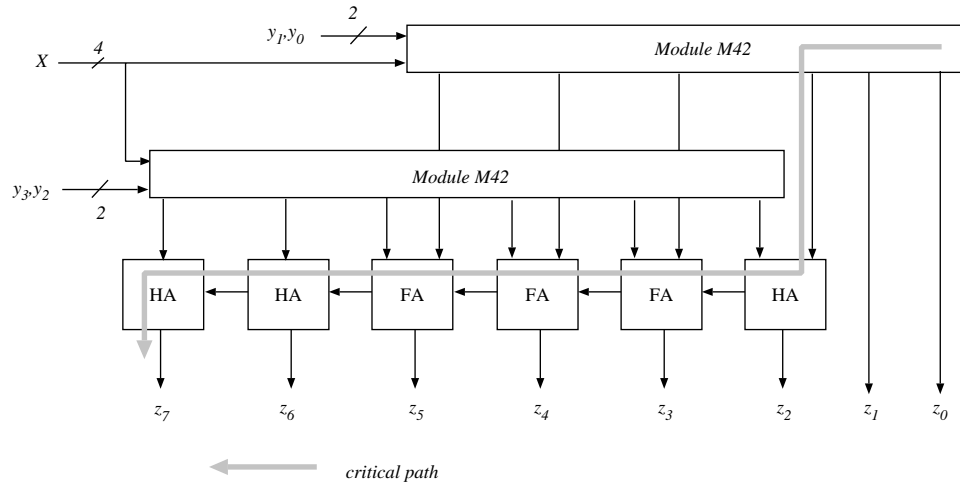b) Using two M42 modules from part a), and extra full-adders (FA) and half-adders (HA), design a 4 by 4 multiplier. Show clearly all modules and connections. Label the inputs and outputs assuming  $X = (x_3, x_2, x_1, x_0)$  and  $Y = (y_3, y_2, y_1, y_0)$  as inputs and  $Z$  bit-vector as the output. Make the design as fast and simple as possible.



c) Determine the critical path in the 4 by 4 multiplier and its delay. Assume that the low to high and high to low propagation delays are the same. For AND gate, the delay is  $t_g$ . The sum and carry-out delays of the full-adder are  $t_s = t_c = t_f$  and of the half-adder  $t_h$ .

$$T_{critical\_path} = t_g + 4t_h + 4t_f$$

**Problem 8.** (10 points)

Design a sequential system specified by the following state transition and output table using a modulo-8 counter with parallel load as the state register, a 8-to-1 multiplexer for the CNT input and NAND gates. Assume  $LD = CNT'$ . The design must take advantage of the count and parallel mode capabilities of the counter. Show all your work.

	$PS$ $Q_2Q_1Q_0$	Input $x = 0$	Input $x = 1$
$S_0$	000	000,0	001,0
$S_1$	001	000,0	010,0
$S_2$	010	000,0	011,0
$S_3$	011	100,0	011,0
$S_4$	100	101,0	001,0
$S_5$	101	000,1	001,0
		$NS, z$	$NS, z$

don't care counter states:  $S_6$  and  $S_7$

$$CNT = S_0x + S_1x + S_2x + S_3x' + S_4x' \quad LD = CNT'$$

$$I_2I_1I_0$$

$$000 \quad \text{if } S_1x' + S_5x' + S_0x'$$

$$001 \quad \text{if } S_4x + S_5x$$

$$011 \quad \text{if } S_3x$$

$$I_2 = 0 \quad I_1 = S_3x = Q_1Q_0x \quad I_0 = (Q_2 + Q_1Q_0)x \quad z = Q_2Q_0x'$$

