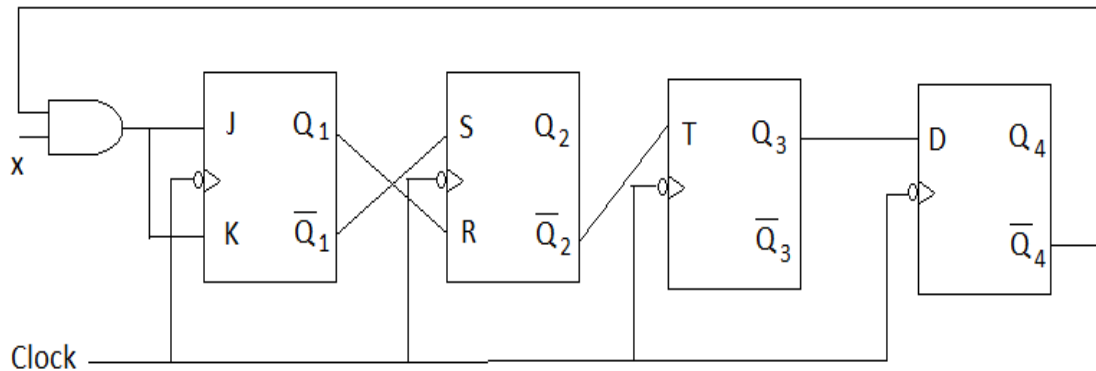



**Paper ID (EL114)****DIGITAL LOGIC DESIGN (EL 114)****B.Tech 2<sup>nd</sup> Semester (2015-16)****Time: 03 Hours****Maximum Marks: 60****Answer all the questions.**

1. Obtain truth table of a combinational circuit which takes a BCD digit (A,B,C,D) and gives excess-3 codes (E,F,G,H). Assume that all the non-BCD numbers give don't care output. Obtain the simplest PLA implementation of the Boolean functions E,F,G and H which uses minimum number of product terms. (8)
2. Suppose two two-bit numbers,  $B_1B_0$  and  $A_1A_0$ , are to be compared. The comparator will have three outputs:  $B=A$ ,  $B>A$  and  $B<A$ . Assume that A and B are unsigned positive integers. Design the comparator using a suitable PAL with minimum number of AND gates. (8)
3. For the following figure, draw the timing diagram for the outputs of each flip-flop for the input sequence  $X=110010$ . Assume that all flip-flops are initially 0. (8)




4. Design a counter using T flip-flops for the following repeated binary sequence: 0,3,1,6,4. Assume that counter will return to 0 from all unused states. (8)
5. For the following problem show a state diagram and a state transition table, and then implement the system using D flip-flop.  
Design a Mealy system whose output is 1 iff the last four inputs were 1001. Assume that overlapping is allowed. (8)

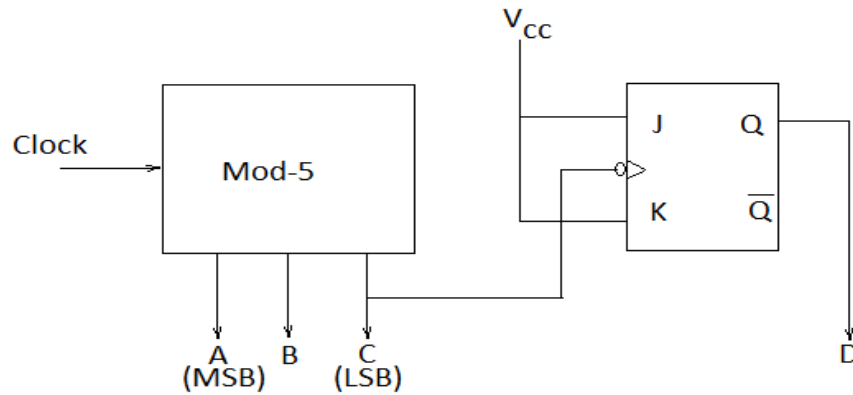6. Consider the following circuit with a binary Mod-5 ripple counter and a JK flip-flop as shown below. Find the modulus of the resulting counter with outputs A,B,C,D and draw the wave forms. (8)



 7. A 4-bit R-2R ladder-type DAC with non-inverting amplifier is shown in the figure below. Determine the output voltage  $V_0$ . (6)



8. The output of a 3-bit Johnson counter is fed to a D/A converter as shown below. Assume that the outputs of the counter are cleared initially. Draw the waveform of  $V_0$  for a complete count sequence of the Johnson counter. Assume that maximum value of  $V_0$  for  $Q_2Q_1Q_0=111$  is 7 volts. (6)

