

Paper ID (EL114)

DIGITAL LOGIC DESIGN (EL 114)

B.Tech 2nd Semester (2015-16)

Time: 02 Hours

Maximum Marks: 40


Instructions to the candidates:

- a) Section A is compulsory.
- b) Answer any two questions from Section B.


Section A

1. Answer all the questions. (10×2)

 - i) Consider the following figure. If $X=0$ and $Y=1$, then will the LED glow? Justify your answer.



 - ii) If $Y = A + \bar{B}$ and $Z = \bar{A} \cdot B$, then what is the relation between Y and Z.
- iii) If $(X)_{\bar{2}}$ represents 2's complement of X, then prove that $((X)_{\bar{2}})_{\bar{2}} = X$.
- iv) Design a digital system to add one with a 4-bit binary number $a_3 a_2 a_1 a_0$ using four half-adders.
- v) $\sqrt{121} = 11$ is correct for at least one number system. Determine the possible radices.
- vi) What is the expression of the output F for the following figure?




- vii) Convert Gray code 100101 to the corresponding binary number.

- viii) 1011 is a 5421 BCD number. What is its decimal value?
- ix) Convert $(2F.1)_{16}$ to octal.
- x) Express the following function into canonical sum-of-products form.

$$F(A, B, C, D) = \bar{A}$$

Section B

 2. (5+3+2)
- i) Draw and explain the operation of the TTL NAND.
 - ii) Write a Boolean expression for Z in terms of A, B, C, D and E.



- iii) Using theorems of Boolean algebra prove that

$$A \cdot B + A \cdot \bar{B} + \bar{A} \cdot B = A + B$$

3. ((2+2)+4+2)

- i) Add the following numbers in binary number system with 2's complement:
 - a) $(14)_{10} + (-25)_{10}$
 - b) $(-20)_{10} + (-17)_{10}$
- ii) Using a Karnaugh map, write simple sum of products expression for F, where $F = \bar{A} \cdot \bar{D} \cdot B + B \cdot \bar{C}$ and $A \cdot B \cdot C \cdot \bar{D}$ is a don't-care state. Then implement the above function using NAND gates.
- iii) Design a combinational circuit with three inputs (A, B, C) and one output F. The output is 1 when $A + C = 0$ or $AC = 1$; otherwise the output is 0. Draw a logic diagram using a single logic gate.

4. (5+5)
- i) Write the truth table of the binary full adder and simplify it using K-map and realize that using NAND gates.
 - ii) Design a combinational circuit that accepts a 4-bit binary number and generates the corresponding 4-bit Gray code.