

Introduction to Digital Design

SAMPLE FINAL EXAM

– closed books and notes –

(8 problems, 180 minutes)

PLEASE BE SYSTEMATIC, ORGANIZED, and NEAT:

– this will be considered in the grading.

Name: _____

Problem	Points	Score
1	10	
2	8	
3	10	
4	14	
5	10	
6	8	
7	10	
8	10	
Total	80	

Problem 1. (10 points)

a) Give a state diagram and state/output table of a Mealy machine which implements the following behavior:

$$z(t) = \begin{cases} x'(t) & \text{if } x(t) = 0 \text{ and } x(k) = 0 \text{ for all } k < t \\ 0 & \text{if } x(t) = 1 \text{ and } x(k) = 0 \text{ for all } k < t \\ x(t) & \text{otherwise} \end{cases} \quad (1)$$

b) Illustrate the time behavior for the input sequence shown bellow. Assume that $x(k) = 0$ for $k < 0$.

t	0	1	2	3	4	5	6
$x(t)$	0	0	1	0	1	1	0
$z(t)$							


c) Is this a finite-memory system? Explain your answer.

Problem 2. (8 points)

Find an equivalent finite state machine with a minimum number of states. Show all partitions and the minimal state table.

PS	$x = 0$	$x = 1$
A	E,0	C,0
B	C,0	A,0
C	B,0	G,0
D	G,0	A,0
E	F,1	B,0
F	E,0	D,0
G	D,0	G,0

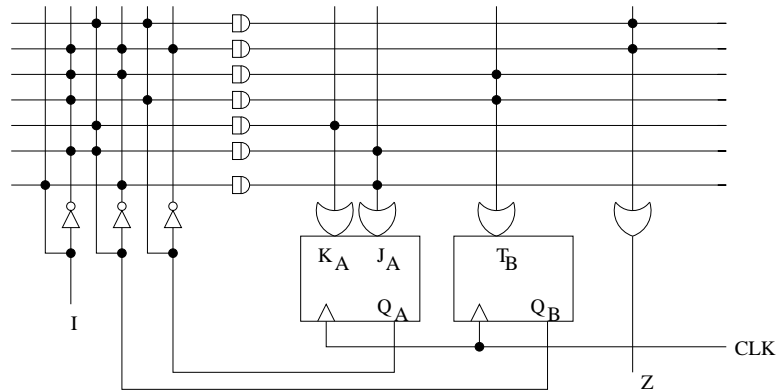Problem 3. (10 points) Derive the state transition/output table for the implementation of the finite state machine shown in the figure below. The next state and output functions are implemented by a PLA structure. The machine has one input I and one output Z . Show expressions for the flip-flop inputs.



PS($Q_A Q_B$)	I	J_A	K_A	T_B	NS	Z

Problem 4. (14 points) (a) Design a cyclic counter with the output sequence 0, 1, 3, 7, 6, 4, 0, 1, ... (of period 6) using JK flip-flops and AND, OR, NOT gates if needed. Assume that the input $x = 1$ always. Select a state assignment that is the same as the coding for the output, that is $z(t) = s(t)$. Show the state/output table. Minimize all expressions. Show the logic diagram of the counter.

State/output table:

	Q0			
	<div style="border: 1px solid black; width: 100px; height: 20px; margin: 0 auto;"></div>			
Q2	<div style="border: 1px solid black; width: 100px; height: 20px; margin: 0 auto;"></div>			
	<div style="border: 1px solid black; width: 100px; height: 20px; margin: 0 auto;"></div>			
	Q1			

	Q0			
	<div style="border: 1px solid black; width: 100px; height: 20px; margin: 0 auto;"></div>			
Q2	<div style="border: 1px solid black; width: 100px; height: 20px; margin: 0 auto;"></div>			
	<div style="border: 1px solid black; width: 100px; height: 20px; margin: 0 auto;"></div>			
	Q1			

	Q0			
	<div style="border: 1px solid black; width: 100px; height: 20px; margin: 0 auto;"></div>			
Q2	<div style="border: 1px solid black; width: 100px; height: 20px; margin: 0 auto;"></div>			
	<div style="border: 1px solid black; width: 100px; height: 20px; margin: 0 auto;"></div>			
	Q1			

$J_0 =$ _____

$K_0 =$ _____

$J_1 =$ _____

$K_1 =$ _____

$J_2 =$ _____

$K_2 =$ _____

Problem 4 (cont.) (b) Design the cyclic counter defined in part (a) using the "one flip-flop per state" approach with D flip-flops. To obtain the output, use a 8-input binary encoder. Show all connections. How is the counter initialized?

Problem 5. (10 points) Design a combinational network that finds the largest and the second largest of four nonnegative integers A, B, C, D . Each integer is represented by four bits. You may use only the following module types: 4×2 -input multiplexer and four-bit comparator. The two-bit output of the comparator is $z = (z_1, z_0)$. If the first integer is larger than the second, the output is $z = 10$. If the second number is larger, the output is $z = 01$ and if the numbers are equal, the output is $z = 00$). Indicate all inputs and connections on the modules being used.

Problem 6. (8 points)

a) Complete the following table assuming true-and-complement number systems. If there is a problem in completing the table, explain. All implicit and explicit values are given in the decimal number system.

Number system	Number of digits n	Signed integer x	Representation value x_R	Digit-vector X
2's compl.	7	-39		
1s' compl.	8		167	
2's compl.				100100100
2's compl.	6	-43		

b) Compute $z = a + 2b - c$ in 2's complement for $a = -7$, $b = 12$, and $c = -97$. Perform calculations on bit-vectors representing a , b and c and show every step of your work. How many bits should z have to represent the correct result? Check your work by showing, for each step, the corresponding values in decimal number system.

Problem 7. (10 points)

- a) Design a 4-bit by 2-bit multiplier module M42. The operands are positive: the multiplicand is $X = (x_3, x_2, x_1, x_0)$, the multiplier is $Y = (y_1, y_0)$, and the product $p = (p_5, \dots, p_0)$. You are allowed to use AND gates, full-adders (FA) and half-adders (HA) only.
- b) Using two M42 modules from part a), and extra full-adders (FA) and half-adders (HA), design a 4 by 4 multiplier. Show clearly all modules and connections. Label the inputs and outputs assuming $X = (x_3, x_2, x_1, x_0)$ and $Y = (y_3, y_2, y_1, y_0)$ as inputs and Z bit-vector as the output. Make the design as fast and simple as possible.
- c) Determine the critical path in the 4 by 4 multiplier and its delay. Assume that the low to high and high to low propagation delays are the same. For AND gate, the delay is t_g . The sum and carry-out delays of the full-adder are $t_s = t_c = t_f$ and of the half-adder t_h .

Problem 8. (10 points)

Design a sequential system specified by the following state transition and output table using a modulo-8 counter with parallel load as the state register, a 8-to-1 multiplexer for the CNT input and NAND gates. Assume $LD = CNT'$. The design must take advantage of the count and parallel mode capabilities of the counter. Show all your work.

PS $Q_2Q_1Q_0$	Input $x = 0$	Input $x = 1$
000	000,0	001,0
001	000,0	010,0
010	000,0	011,0
011	100,0	011,0
100	101,0	001,0
101	000,1	001,0
	NS, z	NS, z