

Lab-8
EL 114 Digital Logic Design

Notes:

- In your lab-book, write your steps/methods, and the observations/results, including the desired vs. the observed truth-table values, etc
 - Get TA's signature after completing each question.
-

1. Using ICs, implement a one-bit Full-adder, as shown in Fig. 1. The full adder has three binary inputs (x , y , z), where z represents the carry-in, and has two binary outputs S and C , where C represents the carry-out.

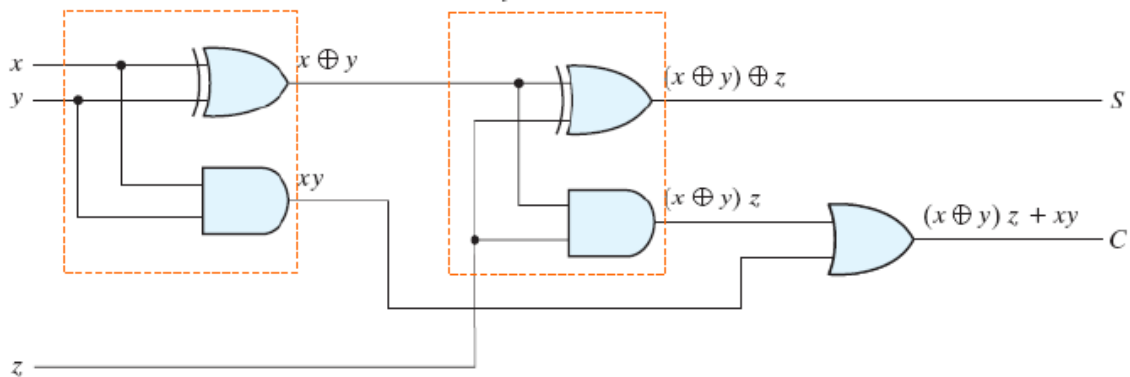


Fig. 1: Full-Adder (FA) using two half-adders

- In your notebook, observe and record the outputs, for all possible combinations of the 3 inputs (i.e. create the truth-table)
2. Using ICs, implement a simple 2-to-4 decoder, using four 2-input AND gates, and some inverters.
 - Draw the circuit in your notebook. (Assume A_1 , A_0 , as the inputs, and D_0 to D_3 as the outputs)
 - Observe and record the output for all possible input combinations. Create an appropriate truth-table for the same in your notebook.
 - Continue to the next question; Do NOT disconnect / disassemble your decoder circuit...
 3. Using the decoder circuit you already built, and using some additional OR gates, implement the following Boolean functions
$$F_1 = A_1' A_0 + A_1 A_0'$$
$$F_2 = A_1 A_0 + A_1' A_0'$$

- Observe and record the outputs for all possible input combinations for the two functions F_1 , and F_2 . Create/observe the appropriate truth-table for the same in your notebook.
4. Using ICs, implement a 1-to-2 decoder with Enable, using 2-input AND gates, and inverters.
- Draw the circuit in your notebook.
 - Observe and record the output for all possible input combinations. Create an appropriate truth-table for the same in your notebook.