 


COMPUTER SYSTEM ORGANISATION

Naresh Jotwani

PowerPoint Slides



PROPRIETARY MATERIAL. © 2010 The McGraw-Hill Companies, Inc. All rights reserved. No part of this PowerPoint slide may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this PowerPoint slide, you are using it without permission.

CHAPTER 3

HARDWARE BUILDING BLOCKS

Electronics

- Electron - an elementary particle
 - indivisible constituent of all matter
 - extremely light and electrically charged
- Movement of electrons through a medium generates electric *current*

- Electrons can also be made to bunch up together without moving, to create electric potential or *voltage*
- Electronics uses properties of electrons as well as various materials to achieve many different useful effects.
- Materials: conductors, insulators, semiconductors


Digital Electronics

Utilizes two distinct states of an electronic device, to provide a physical realization of the notion of *one bit of information*


Allows us to build an electronic system in which a large number of bits can be reliably stored, written as input, or read as output

Also allows us to build a system for *processing* the information stored, according to well-defined instructions (i.e. program) provided by the user

Simple “ON-OFF” switch

 

 (a) Switch is ON. Voltage at point X is 5 volts.



(a) Switch is OFF. Voltage at point X is 0 volts.

An ON-OFF switch and its two possible output voltages. A *transistor* is the electronic device which functions as a switch.

- To achieve electronic storage of a large number of bits, transistors are arranged in a rectangular array, or grid.
- At each intersection of a row and a column in this grid, a single bit of storage is provided.
- Appropriate means have to be provided to *read* or *write* any single bit in this grid.
- A typical semiconductor memory element is built on such a principle.

Logic Gates

- (i) *and* operation, also known as *conjunction*, has output 1 if and only if all of its inputs have value 1.
- (ii) *or* operation, also known as *disjunction*, has output 1 if and only if at least one of its inputs has value 1.
- (iii) unary *not* operation, also known as negation, has output 1 if and only if input is 0, and *vice versa*.
- By using a combination of these operations, we can define other complex functions.
- Electronic circuits implementing these operations are known as *logic gates*.

Value of input X_1	Value of input X_2	Value of output Y
0	0	0
0	1	0
1	0	0
1	1	1

 


Table and graphical notation of *and* operation

Value of input X_1	Value of input X_2	Value of output Y
0	0	0
0	1	0
1	0	0
1	1	1

 


Table and graphical notation of *or*
operation

Combinational Circuits


- Consider a digital circuit with three input variables $X1$, $X2$ and $X3$, and output variable Y , defined using *and*, *or* and *not* gates in the following way:

$$Y = or(X3, and(X1, not(X2)))$$

- Note here that:
 - (i) The output of *not* is one of the inputs of *and*; the second input of *and* is $X1$.
 - (ii) The output of *and* is one of the inputs of *or*; the second input of *or* is $X3$.
- Replacing function notation by *operator* symbols $+$, \cdot , and \neg for functions *or*, *and* & *not* respectively, we get:


$$Y = X3 + X1 \cdot (\neg X2)$$

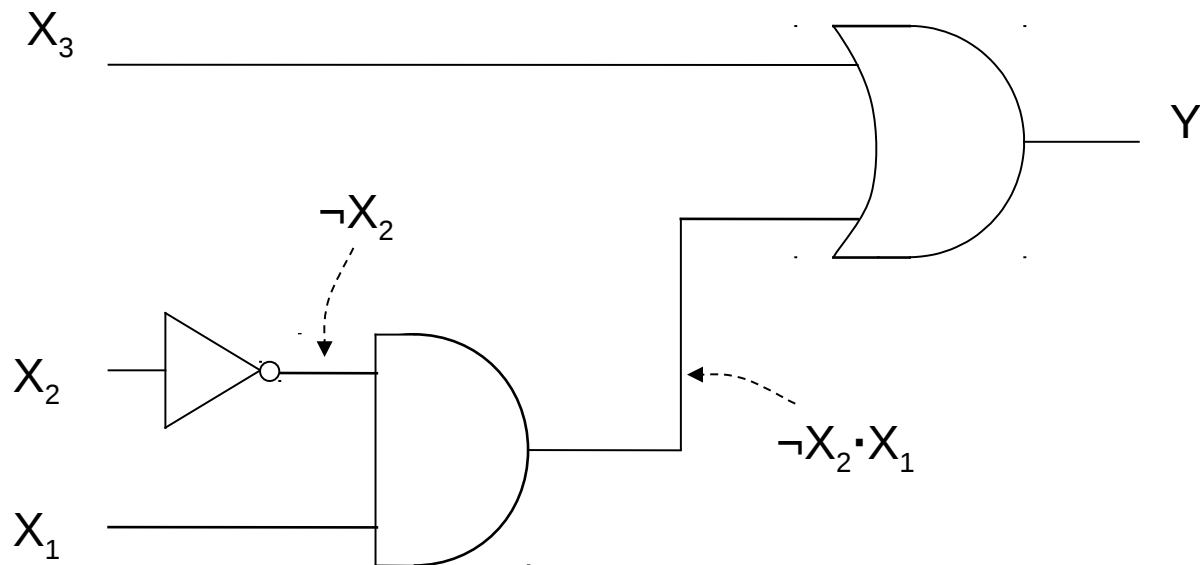The same function can be represented graphically as under, in the form of a *schematic diagram* of a simple digital circuit:



Sequential circuits

 - A combinational function such as $Y = f(X_1, X_2, \dots, X_n)$ has 'no memory', because the output is determined solely by the inputs.
- Typical electronic circuit which can record one bit of information is the *flip-flop*.



A flip-flop with an input line, an output line, and a clock input at the bottom

- Once in every clock cycle, at an appropriate clock *transition* or *edge* – the flip-flop records the state of the input.
- If input is 0 at the clock transition, the flip-flop records 0;
- If input is 1, the flip-flop records 1.
- When a flip-flop is in state 1, it is said to be *set*, and when it is in state 0, it is said to be *reset*.
- A flip-flop thus provides one bit of memory. By arranging N such flip-flops in a linear array, we obtain N bits of memory

SEQUENTIAL CIRCUIT


In the figure, A, B, C and D have the following meaning:

A - Input signals to the sequential circuit

B - State of the circuit at time t

C - Output signals of the sequential circuit

 D - State of the circuit at time $t + \Delta t$



Integrated Circuits


- An IC has components such as transistors, resistors and capacitors created in silicon, with strips of conductors connecting them.
- Electrical isolation between components is achieved by creating insulating layers of silicon dioxide.
- To define required geometries on the silicon substrate, two-dimensional optical masks are placed over it during processing steps.

- A silicon chip with an IC must be provided with *leads* for making connections to other chips and components, and it must be packaged durably in ceramic or plastic.
- ICs are available for a vast range of useful functions, including logic gates, counters, decoders, timers, memory chips, processors, and device controllers.
- Within a computer system, ICs are mounted on *printed circuit boards* (PCBs).

Clock signal

- Majority of circuits employed in today's computer systems employ a clock signal .
- In the next slide, three cycles of a typical clock signal are shown.
- Horizontal axis represents time, while the vertical axis represents clock voltage.

 - In one time period, the clock signal exhibits two *transitions* or *edges*.
- Within one time period, the part of clock signal between the rising edge and the falling edge is known as a *clock pulse*.
- A flip-flop – or in general any sequential circuit – utilizes one of the two edges of a clock pulse as an instant of transition.




- From one *master clock*, circuit designers can derive other lower frequency clocks.
 - Thus different parts of a computer system can operate at different clock speeds, if required
- Any processing step in a computer system happens at the rising or falling edge of a clock pulse.
- It is important to view the clock signal as a *physical signal*, and not a logical signal.
- Several manufacturers have specialized clock generator circuits in their product line, which system designers can use as building blocks.

Registers


- When an array of N flip-flops is designed as a single unit of storage, we call the resulting element an *N -bit register*.
- If a register is used primarily as a counter, we may call it an *N -bit counter*.
- The unsigned integer count in an N -bit counter goes from 0 to $2^N - 1$, after which it is again reset to 0.

A bank of eight N -bit registers

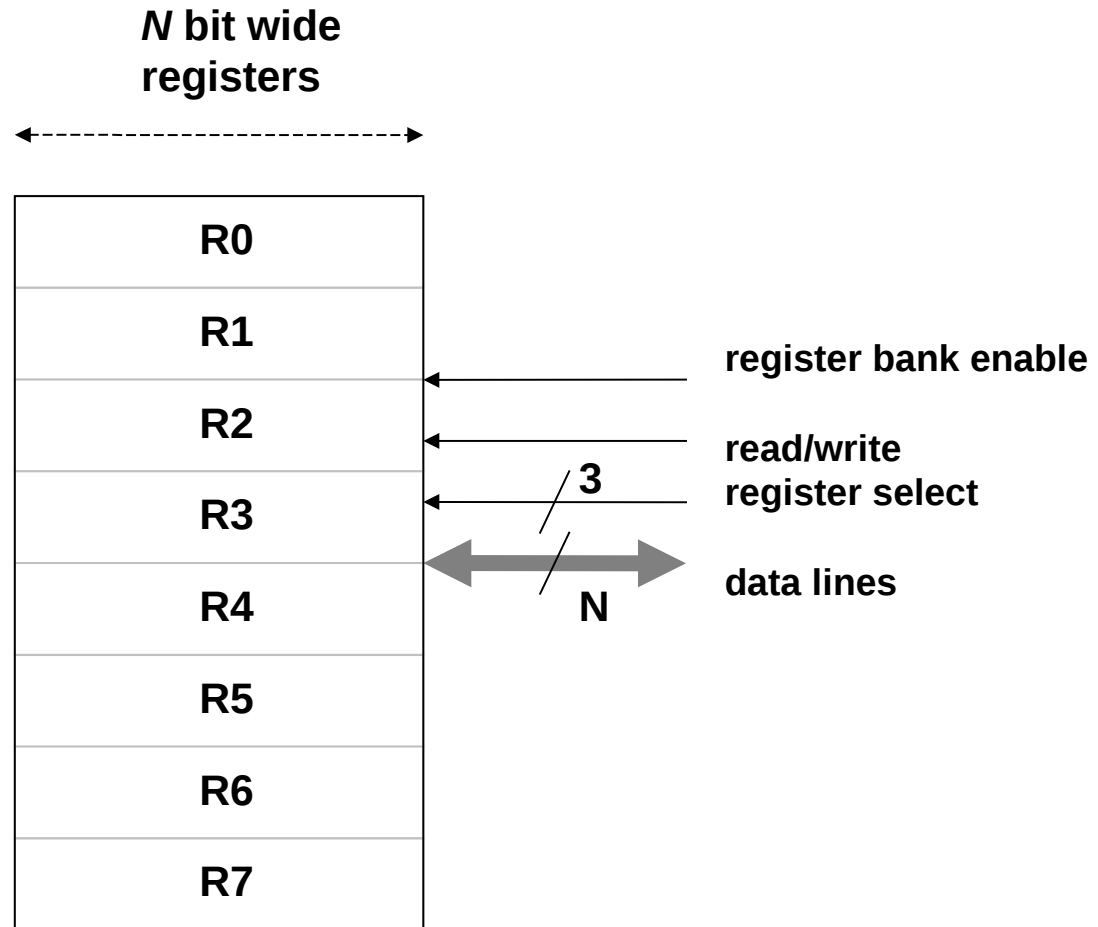

- In the previous slide, the thick line shows *bi-directional data lines*
 - They connect this register bank with some other part of the system
- Above the data lines, we see a group of three lines labeled *register select*.
 - Any operation on the bank targets one of the eight registers, so we need three bits of information to select a register for a *read* or a *write* operation.
- Above the register select lines, there is a signal line labeled *read/write*.
 - In a given clock cycle, the *read/write* signal decides whether a read or write operation takes place

- At the top, we see a signal labeled *register bank enable*.
 - We must *enable* the register bank only when performing an operation on it, and not otherwise.
- In the previous figure, we read or write N bits in one clock cycle – i.e. the N bits of the selected register are read or written *in parallel*.
- The next slide shows a 16-bit register provided with both parallel and *serial* modes of operation.

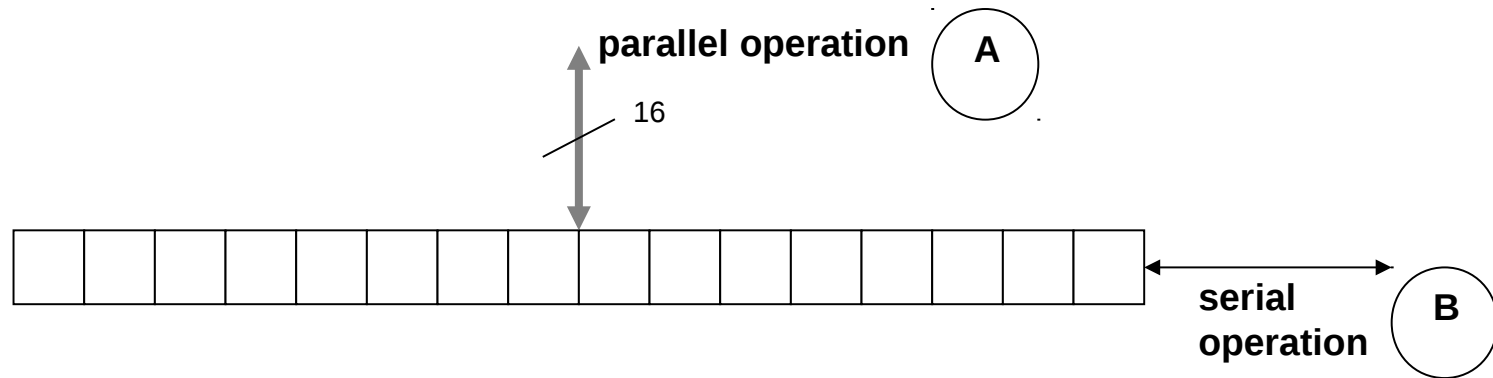

The operation of the above register can be either

- (i) a parallel write at 'A', followed by serial shift of the data out from 'B', or
- (ii) serial shift of the data in from 'B', followed by parallel read at 'A'.

- In serial mode, register bits are read in or written out one bit per clock cycle, in serial order. Shown at point 'B' in the figure; therefore on an N -bit register, a complete serial read or write operation takes N clock cycles.

- Serial mode of data transfer is required if a device exchanges data only in serial mode – i.e. one bit at a time. Most communication links function in this mode.
- Thus, a register such as the one shown above can be operated in either
‘parallel in, serial out’ mode
or
‘serial in, parallel out’ mode.
- A *shift register* is a register whose contents can be shifted left or right by a specified number of bits.


Memory elements

Usually made byte addressable for flexibility and efficiency in programming.

- *Byte addressable*: i.e. every *memory address* points to one eight-bit byte in the memory block.
- For faster operations, often such memory is also made capable of multi-byte operations.

- The next slide shows the logical organization of byte addressable memory.
 - If a word equals four bytes, then every fourth byte of memory occurs at a *word boundary*. Counting memory bytes from 0 onwards, we then have word boundaries at the end of bytes 3, 7, 11, and so on.
 - Word operations on main memory are usually constrained to be aligned with word boundaries, and likewise for *half-word* and *double-word* operations.
- Any random byte or word in such a memory element can be accessed in one memory cycle. Therefore such memory is known as *random access memory*, or RAM.

Organization of byte-addressable memory

 


Input and output signals of a typical memory element are shown in the next slide. Note the *address lines*, *data lines*, and the *read/write* signal.

Other requirements:

 - (i) A memory element needs an *enable* signal, and
- (ii) the memory is located at a specific *address*.

An address decoder element is a combinational circuit which generates the required *enable* signal.

This *enable* signal is generated when the higher order address lines have the value determined for this memory element. This results in the memory element being located at a specific address.



Types of memory elements


- Static memory element
 - faster, can hold contents indefinitely, relatively expensive, needs more chip area per bit
 - e.g. processor cache memory, register bank
- Dynamic memory element
 - relatively slower, needs periodic refresh, relatively inexpensive, needs less chip area per bit.
 - used in main memory.

Other useful elements:

- *Data bus* – Connects together the various system elements
- In one *bus cycle*, such a bus carries out a complete data transfer operation between any two elements connected to it.
- A typical bus may consist of data lines, address lines, read/write signal, various other control signals, clock signal, supply voltage, and ground.

- As seen above, address lines need to be decoded to generate the *enable* signal for a memory element.
- *Decoder* ICs simplify this work.
- The next slide shows a schematic diagram of the *3-to-8 decoder*
- The three inputs to such a decoder will have one of $2^3 = 8$ possible values, viz. 000, 001, 010, 011, 100, 101, 110 and 111.
- Accordingly, exactly one of the eight output lines will have value 1, while all others are 0.

 - Thus the 3-bit binary number on the input determines which single one of the eight outputs has value 1.
- In the diagram, assume that the input & output signals are numbered in increasing order from top to bottom. The next slide shows the truth table of this device.




A 3-to-8 decoder

Inputs d_0, d_1, d_2	Outputs $s_0, s_1, s_2, s_3, s_4, s_5, s_6, s_7$
0, 0, 0	1, 0, 0, 0, 0, 0, 0, 0
0, 0, 1	0, 1, 0, 0, 0, 0, 0, 0
0, 1, 0	0, 0, 1, 0, 0, 0, 0, 0
0, 1, 1	0, 0, 0, 1, 0, 0, 0, 0
1, 0, 0	0, 0, 0, 0, 1, 0, 0, 0
1, 0, 1	0, 0, 0, 0, 0, 1, 0, 0
1, 1, 0	0, 0, 0, 0, 0, 0, 1, 0
1, 1, 1	0, 0, 0, 0, 0, 0, 0, 1

Truth table of the 3-to-8 decoder

- An *encoder* works in a manner which is exactly the converse of the *decoder*.
- An 8-to-3 encoder has eight inputs, exactly one of which must be set to 1 at any time.
- Its three output lines have a value from 000 to 111, depending on which input line is set to 1.

- The encoder must be operated under the constraint that exactly one of its inputs has value 1 at any time.

 


An 8-to-3 encoder

- A *comparator* is a combinational circuit which compares two binary values, say A and B, and generates output according to the result of the comparison.
- The result on the output indicates one of the three possible results of comparison:

$$A < B, A = B, \text{ or } A > B.$$

- A *multiplexer* is a circuit with several sets of inputs, exactly one of which is connected to the outputs, depending on the control signals applied.
- The figure in the next slide shows a 4-line, 4-to-1 multiplexer.

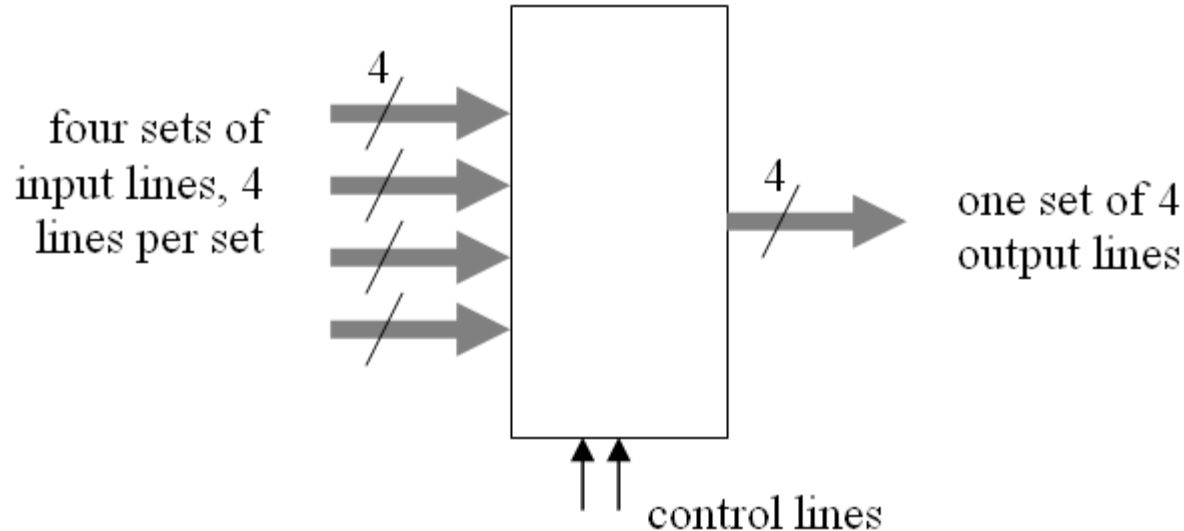- The two control signals shown at the bottom of the device can have value 00, 01, 10 or 11.
- Data from the corresponding set of four input lines appears as the one set of four output lines.



A 4-line, 4-to-1 multiplexer

Truth table of a 4-to-1 multiplexer

Control inputs* c_0, c_1	Output set*
0, 0	= input set A
0, 1	= input set B
1, 0	= input set C
1, 1	= input set D

*Assume that, in the previous figure, control inputs are named c_0 and c_1 , and data input sets are named A, B, C and D as we go from top to bottom


- In a *demultiplexer*, the single set of input lines is connected to exactly one out of several sets of output lines – as determined by the control signals.
- The next slide shows a 4-line, 1-to-4 demultiplexer.

Control inputs* c_0, c_1	Input data appears on output set*
0, 0	A
0, 1	B
1, 0	C
1, 1	D

Truth table of a 1-to-4 demultiplexer

*Assume that, in the next figure, control inputs are named c_0 and c_1 , and output sets are named A, B, C and D as we go from top to bottom.

 
- The two control signals shown at the bottom of the device can have value 00, 01, 10 or 11.
- Accordingly, data from the set of four input lines appears on exactly one of the four sets of output lines.



A 4-line, 1-to-4 demultiplexer

- A set of three 2-to-1 multiplexers can be connected together to achieve the functionality of a 4-to-1 multiplexer.
- This is shown schematically in the next slide.
- The four sets of inputs of the 4-to-1 multiplexer are denoted as A_I , B_I , A_{II} and B_{II} , respectively.
- Input sets A_I and B_I are connected to the inputs of 2-to-1 multiplexer I, while input sets A_{II} and B_{II} are connected to the inputs of multiplexer II.

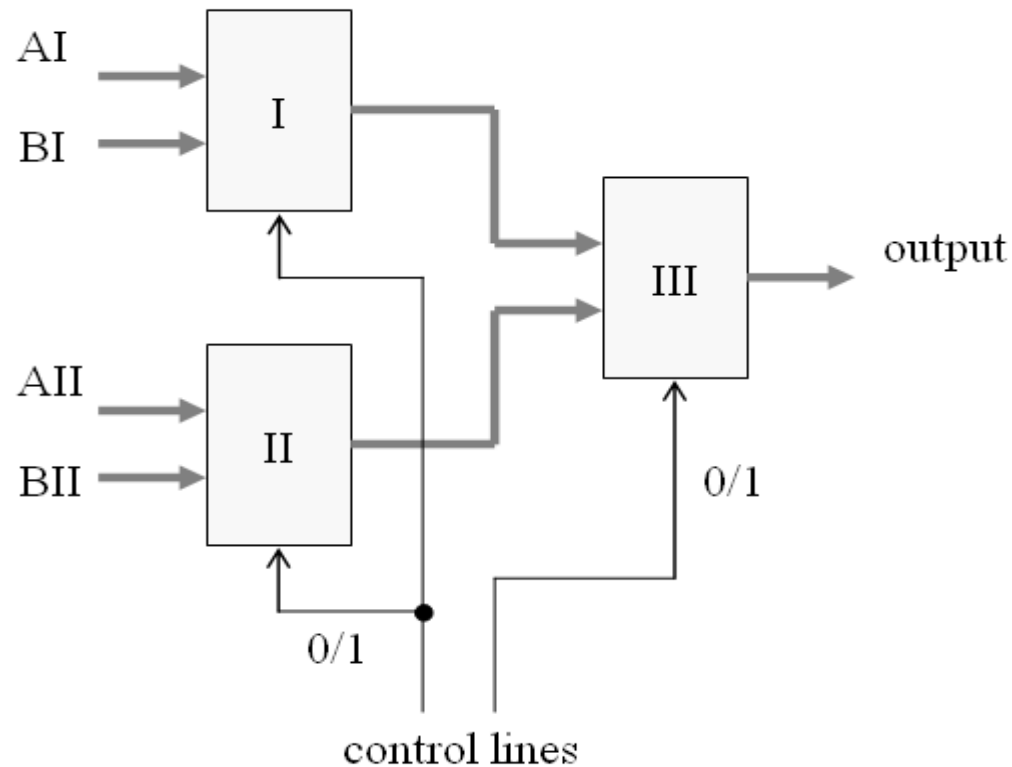- By applying the correct value (0 or 1) to the first control signal, we can select either
 - (i) A_I as the output of I and A_{II} as the output of II, or
 - (ii) B_I as the output of I and B_{II} as the output of II.
- Thus either (i) A_I and A_{II} , or (ii) B_I and B_{II} reach the input of multiplexer III.



Some other useful elements

- A *latch* is a flip-flop employed for capturing a single pulse or transition on a line
- An *8-bit latch* is a similar device with eight flip-flops
- A *buffer* is a device which strengthens the input signals without altering their logical value
- A *timer* device has an internal or external clock. Based on its pre-defined 'timer count', the device generates an output pulse once in that many clock periods

Summary

- *Functional* point of view of Electronic technology – the building blocks of various sub-systems of a computer system
- Basic principles of the transistor serving as an ON-OFF switch, logic gates, combinational circuits, flip flops, and sequential circuits.
- Combinational function implemented using *and*, *or* and *not* gates
- Flip-flop - The basic circuit element which stores one bit of information
- Combinational and sequential circuits
- Integrated circuit technology – VLSI
- Crucial role of the clock signal in computer circuits
- Other useful building blocks of computer systems
 - registers and register banks, memory blocks, encoder, decoder, multiplexer, demultiplexer, and others.