

Time: 2 hr

Maximum marks: 50

READ THE INSTRUCTIONS CAREFULLY:

1. START EACH ANSWER IN A NEW PAGE.
2. MAKE PROPER ASSUMPTIONS WHERE NECESSARY.
3. CALCULATORS ALLOWED.
4. IN CASE OF ANY QUERY, MENTION IN THE PAPER AND WITH PROPER SUPPOSITIONS / ASSUMPTIONS PROCEED WITH THE EXAMPLE. MENTION WHAT YOU SUPPOSE CLEARLY.


**Question 1**

**10 Marks**

Determine, for the emitter-follower network of figure below,

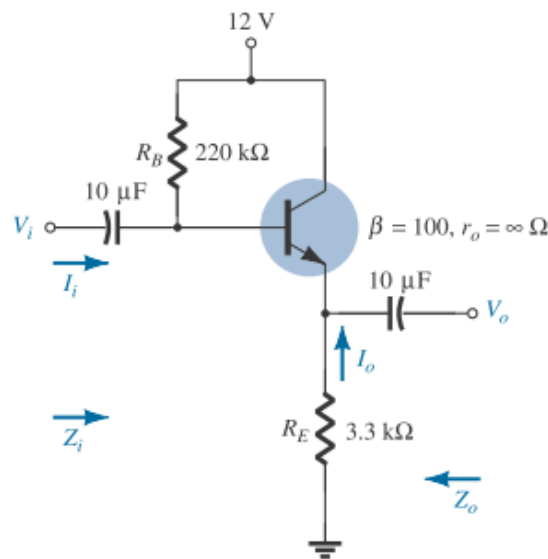- a.  $r_e$
- b.  $Z_i$
- c.  $Z_o$
- d.  $A_v$
- e. Repeat parts (b) through (d) with  $r_o = 25 \text{ k}\Omega$  and compare results.


Here  $Z_i$  and  $Z_o$  are input and output impedances or resistances.



OR

Determine for the below network:

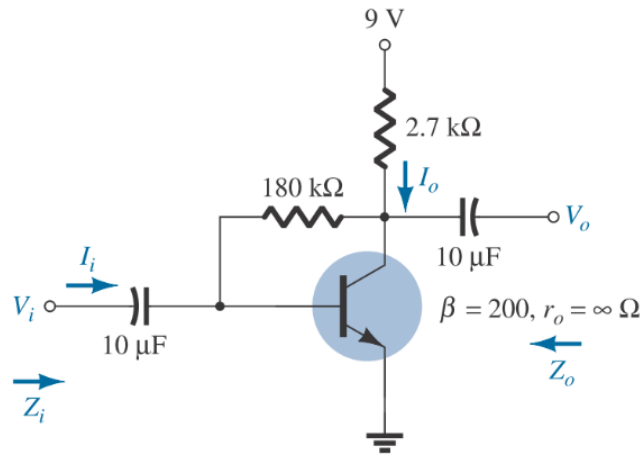- $r_e$
- $Z_i$
- $Z_o$
- $A_v$
- Repeat parts (b) through (d) with  $r_o = 20 \text{ k}\Omega$  and compare results.




## Question 2

8 Marks

Determine for the below network:


- $r_e$
- $Z_i$
- $Z_o$
- $A_v$
- $A_i$

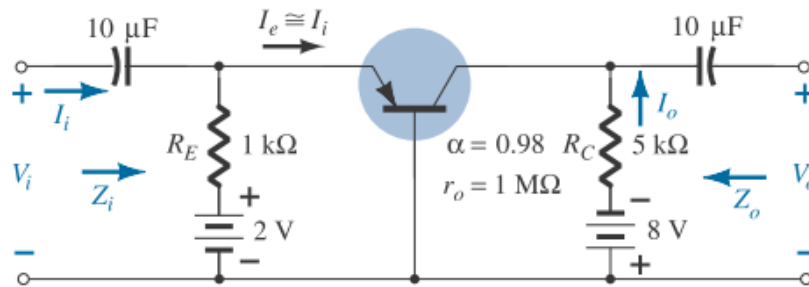
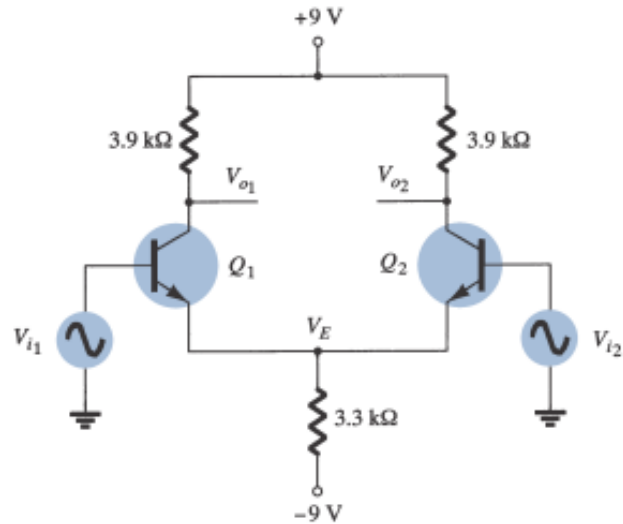
## Question 3

5 + 5 Marks

I For the below circuit, calculate the DC voltages and currents.




II Design circuit to provide outputs that are 10, 20 and 50 times larger than the input by connecting three operational amplifier stages. Use a feedback resistor of  $R_f = 500 \text{ k}\Omega$  in all the stages.

#### Question 4

10 Marks

Determine the lower cutoff frequency for the below network using the following parameters:
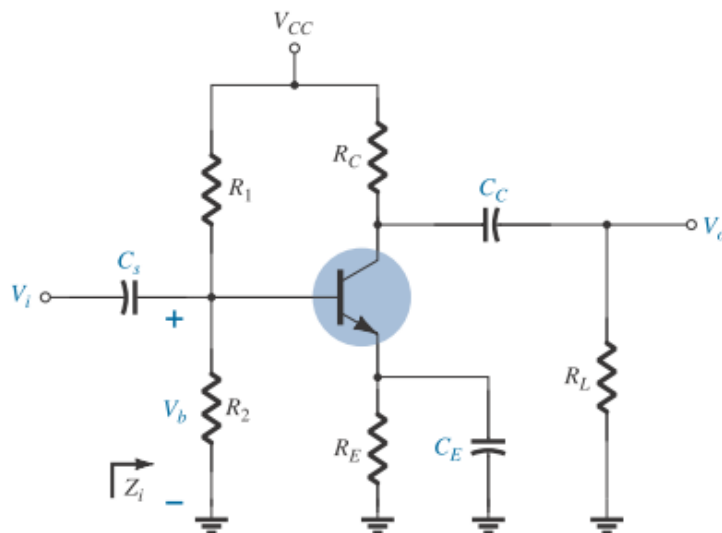
$$\begin{aligned}
 C_s &= 10 \mu\text{F}, & C_E &= 20 \mu\text{F}, & C_C &= 1 \mu\text{F} \\
 R_1 &= 40 \text{ k}\Omega, & R_2 &= 10 \text{ k}\Omega, & R_E &= 2 \text{ k}\Omega, & R_C &= 4 \text{ k}\Omega, \\
 R_L &= 2.2 \text{ k}\Omega \\
 \beta &= 100, & r_o &= \infty \Omega, & V_{CC} &= 20 \text{ V}
 \end{aligned}$$




Repeat the analysis with a source resistance  $R_S$  of  $1\text{k}\Omega$ . The gain of interest will now be  $V_o / V_S$  rather than  $V_o / V_i$ . Compare results.

### Question 5

12 Marks

In the two-stage feedback amplifier shown, the transistors are identical and have the following parameters:  $\beta = 50$ ,  $r_{\pi} = 2\text{K}$ . Calculate for **any one circuit**:

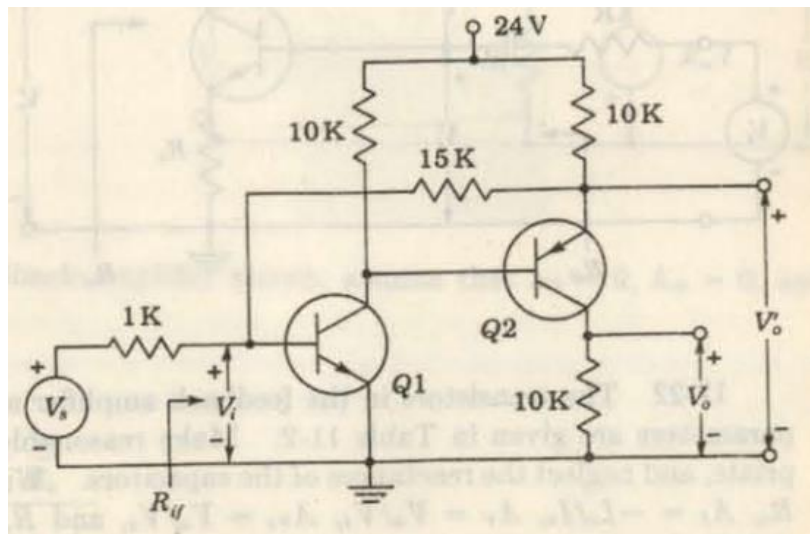- $A'_v = V'_o / V_i$
- $R_{if}$
- $A_v = V_o / V_i$
- $A_{vf} = V_o / V_S$



OR

