

## Lab 9

### EL 114 Digital Logic Design


Notes:

- In your lab-book, remember to write your steps/methods, and the observations/results
  - Get TA's signature after completing each question.
- 



- All the following questions are to be done in Logisim.
- Make sure you draw each new schematic using "Add circuit" option in the Project menu, so that you can later make use of the instances of that particular schematic/circuit to build larger schematics.

1. Design clocked S-R, J-K, D and T flip-flops using NAND gates and write their corresponding truth tables.
2. Determine the count sequences of the following counters.

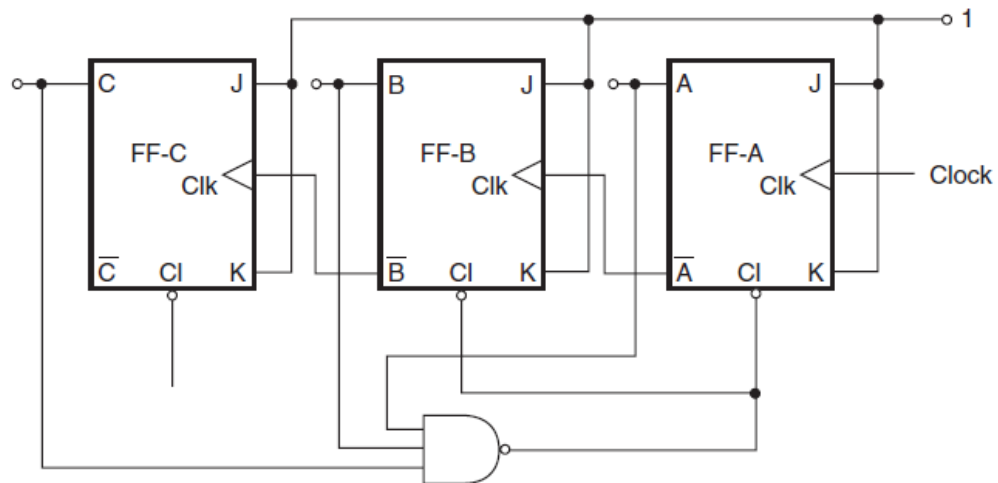
- a) For the following figure, write the sequence of the output states observed on C (MSB), B and A starting with all the flip-flops cleared.



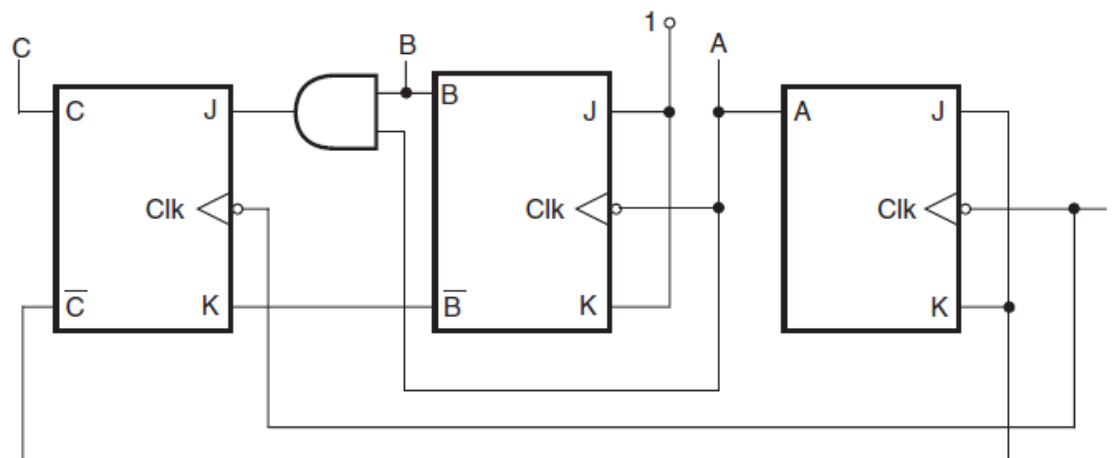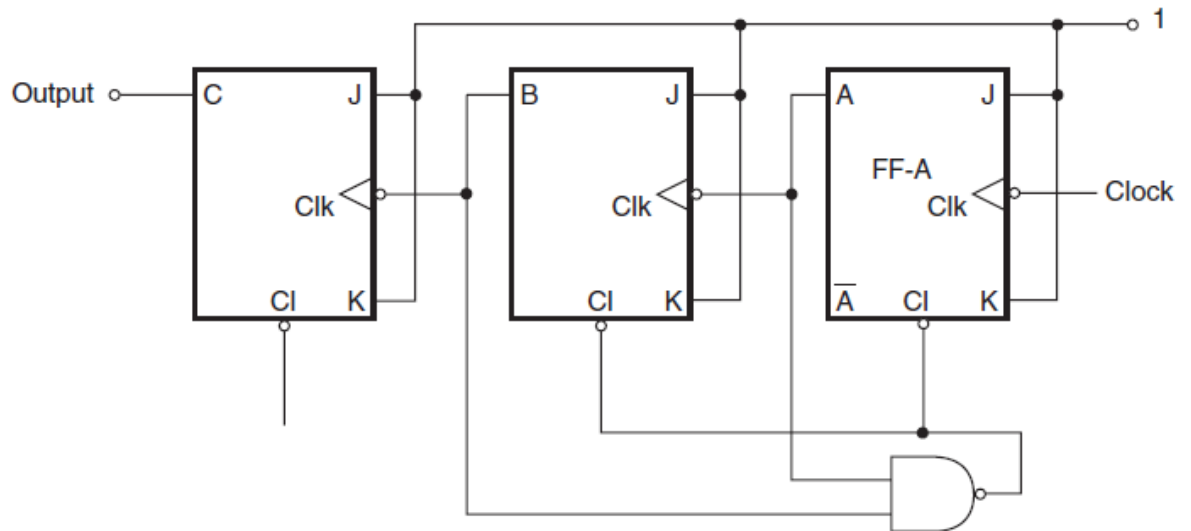- c) For the following figure, write the sequence of the output states observed on C (MSB), B and A starting with all the flip-flops cleared.



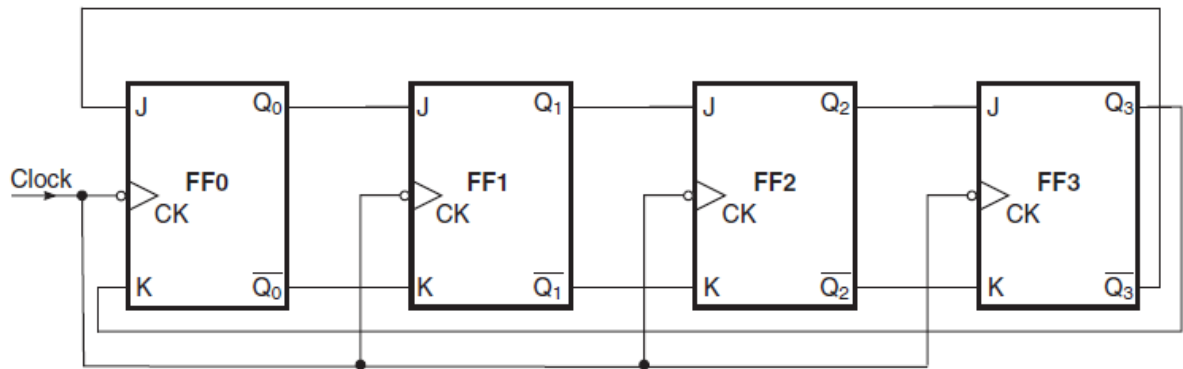- d) For the following figure, write the sequence of the output states observed on  $Q_3$  (MSB),  $Q_2$ ,  $Q_1$  and  $Q_0$  starting with all the flip-flops cleared.



- e) For the following figure, write the sequence of the output states observed on C (MSB), B and A starting with all the flip-flops cleared.

